

Design And Implementation Of 4-Bit Flash ADC

Aparna P. Pawar
Electronics and Communication
KLS VEDIT
Haliyal, India

Manjula Doddabasappa Karisiri
Electronics and Communication
KLS VEDIT
Haliyal, India

Naveena C. Kashigar
Electronics and Communication
KLS VEDIT
Haliyal, India

Shivaleela S. Kusugal
Electronics and Communication
KLS VEDIT Haliyal, India

Prof. A. V. Kolaki
Asst. Professor
Electronics and Communication
KLS VEDIT Haliyal, India

Abstract— Analog-to-Digital Converters (ADCs) play a crucial role in modern electronic systems by transforming real-world analog signals into digital data for further processing. Among the various ADC architectures, the Flash ADC is particularly notable for its exceptionally fast conversion speed, making it ideal for applications that demand real-time performance, such as high-speed data communication and signal acquisition systems. However, the inherent use of numerous comparators in Flash ADCs leads to increased power consumption and design complexity.

This paper presents the design and simulation of a 4-bit Flash ADC using 180nm CMOS technology, developed and analyzed within the Cadence EDA environment. The study provides valuable insights into the practical aspects of implementing high-speed, power-aware mixed-signal circuits, offering guidance for designers working on performance-critical systems.

Keywords— Flash ADC, Resistor ladder, Comparator, Encoder

I. INTRODUCTION

Analog-to-Digital Converters (ADCs) serve as vital components in bridging the analog and digital domains of electronic systems. Their primary function is to convert continuous-time analog signals into digital values, enabling further processing by digital logic. Among the various ADC architectures, the Flash ADC is recognized for its rapid conversion speed, made possible by its parallel structure. In the case of 4-bit Flash ADC, the analog input is mapped to one of 16 discrete levels, making it ideal for applications requiring conversion delay.

The architecture of a Flash ADC typically includes three main components: a reference ladder that generates uniformly spaced voltages, an array of comparators that evaluates the input signal against these reference levels, and a digital encoder that transforms the comparator outputs (thermometer code) into binary format. However, the number of comparators required increases exponentially with resolution, which leads to greater power usage, silicon area, and design complexity. For these reasons, Flash ADCs are generally implemented in low- to moderate-resolution designs (typically 4–6 bits) where speed is the primary concern.

This paper presents the design and simulation of a 4-bit Flash ADC using Cadence tools and 180nm CMOS technology. Key design metrics such as speed, power efficiency, and layout area are evaluated to guide the development of optimized high-performance analog-to-digital conversion systems.

The architecture of a flash ADC consists of three main blocks:

Reference Ladder (Voltage Divider Network): This generates a set of equally spaced reference voltages using a resistor or capacitor ladder. For a 4-bit ADC, the ladder generates 15 reference voltages corresponding to the 16 digital output levels.

Comparator: A set of 15 comparators is used to compare the input analog voltage to each reference voltage. The outputs of these comparators produce a thermometer code—an intermediate code representing the input level.

Encoder: Once the thermometer code is generated by the comparator array, it is passed through a digital priority encoder that translates the sequence into a 4-bit binary output, representing the corresponding quantization level.

Despite the speed advantages of Flash ADCs, they present certain limitations. One key drawback is scalability. As resolution increases, the number of required comparators grows exponentially—specifically, an n -bit Flash ADC needs $2^n - 1$ comparators. This rapid growth results in greater silicon area usage, higher power consumption, and added circuit complexity. As a result, Flash ADCs are generally reserved for low to moderate resolutions, typically between 4 and 6 bits, where high-speed performance is essential and the trade-offs are manageable.

In this project, the design of a 4-bit Flash ADC is carried out using Cadence tools in 180nm CMOS technology. The design focuses on optimizing key performance parameters such as speed, power consumption, and area, providing insights into the practical implementation of high-speed ADCs in mixed-signal systems.

II. LITERATURE REVIEW

Sam et al. [1] proposed a low-power design featuring an open-loop comparator and a multiplexer-based encoder. Implemented using 90nm CMOS in the Cadence environment, their approach removed traditional priority encoders, resulting in reduced circuit complexity and power consumption, with operation at 100 MHz and a power requirement of just 0.265 mW.

Razavi et al. [2] introduced a Threshold Inverter Quantization (TIQ)-based ADC architecture, replacing resistor ladders with inverter switching thresholds. Additionally, they used reversible logic for encoding, significantly lowering power dissipation. Fabricated in TSMC 180nm CMOS, their ADC achieved 2 GS/s operation with a power consumption of only 330 μ W.

Gupta et al. [3] focused on a voltage-scalable Flash ADC using capacitive feedback and dynamic voltage scaling techniques. Their approach eliminated resistive reference ladders and included a feedback mechanism for improved linearity and power efficiency, making it suitable for low-voltage SoC applications.

In another notable work, Nasri et al. [4] combined folding and flash architectures to balance speed and area efficiency. Their design, developed in 65nm CMOS, achieved 1 GS/s with a power consumption of 700 μ W and a Signal-to-Noise and Distortion Ratio (SNDR) of 22.3 dB at 100 MHz, showcasing its effectiveness for high-speed wireless applications.

Kim et al. [5] presented a 4-bit Flash ADC fabricated in 90nm CMOS, emphasizing layout optimization and offset calibration. Their architecture, capable of operating at 3.5 GS/s, utilized compact analog blocks and minimized comparator mismatch, making it a strong candidate for ultra-fast communication systems.

Torfs et al. [6] addressed power consumption in a 4-bit Flash ADC designed for ranging applications. Implemented in 180nm CMOS, their design achieved a 700 MS/s sampling rate while maintaining 4.43 mW power consumption. By reducing comparator kickback noise and enhancing calibration, they achieved a figure of merit (FoM) of 0.46 pJ per conversion step—the lowest reported for its category at the time.

III. METHODOLOGY

The 4-bit Flash ADC was developed using a structured, step-by-step methodology with a focus on achieving high-speed data conversion while maintaining energy efficiency. The design flow began with architectural planning, followed by schematic-level circuit design, layout creation, and post-layout simulation. This process was carried out using Cadence Virtuoso, a widely adopted EDA platform, in conjunction with 180nm CMOS technology, which strikes a practical balance between performance and area in analog design.

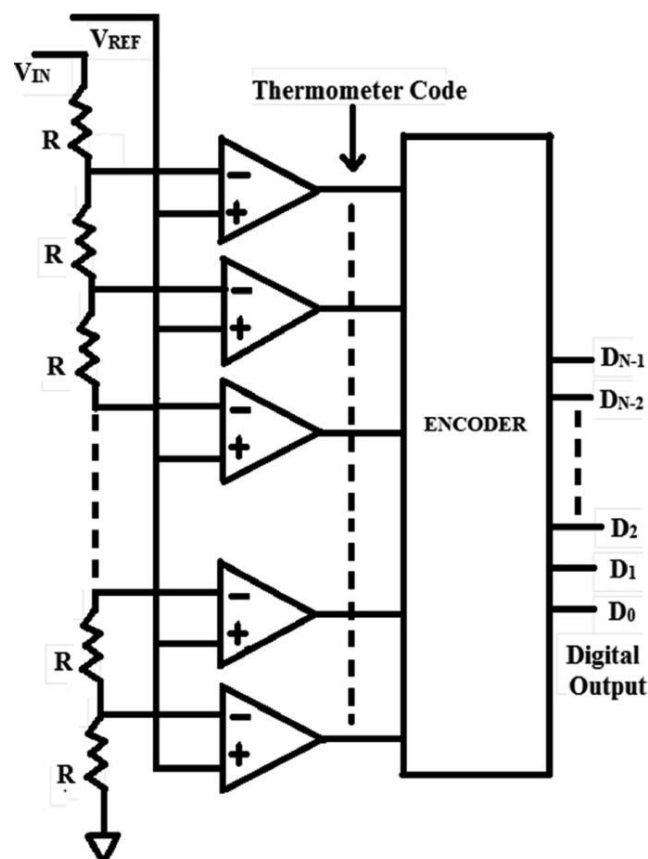


Fig No 1 Block Diagram of 4-Bit Flash ADC

Figure 1 illustrates the system architecture of the Flash ADC, which includes three fundamental building blocks: the resistor ladder, the comparator array, and the digital encoder.

Resistor Ladder Network: The analog input voltage V_{IN} is compared against a series of predefined threshold levels generated by a resistor ladder network. This ladder is constructed using equal-value resistors connected in sequence between a reference voltage V_{REF} and ground. The voltage at each node between resistors forms a unique reference point for one comparator.

Comparator Array: Each comparator receives the analog input V_{IN} and one of the reference voltages from the ladder. If V_{IN} exceeds the reference level, the comparator outputs a logic high ('1'); otherwise, it outputs a logic low ('0'). The result is a thermometer code—essentially a sequence of ones followed by zeros that indicates how many thresholds have been surpassed by the input signal.

Thermometer-to-Binary Encoder: The output of the comparators is passed to an encoder that interprets the thermometer code and converts it into a binary format. For a 4-bit ADC, the encoder generates four output bits (D_3 through D_0) that represent the digital equivalent of the input voltage. This conversion enables fast, parallel processing suitable for high-speed applications.

Digital Output: The final digital output is a binary word proportional to the input voltage level, completing the analog-to-digital conversion process.

IV. IMPLEMENTATION

In this project, a 4-bit Flash ADC was designed and implemented using a structured approach, with an emphasis on clarity, speed, and design efficiency. The process begins with the construction of a resistor ladder network, which generates a set of evenly spaced reference voltages. For a 4-bit resolution, the ladder comprises 16 resistors of equal value connected in series between a supply reference voltage V_{ref} and ground. This configuration creates 15 intermediate voltage levels, which serve as comparison thresholds.

A bank of 15 comparators is then used to evaluate the input signal V_{in} against these reference voltages. In this design, each comparator takes the analog input on its non-inverting terminal and a unique reference voltage on the inverting terminal. When the input voltage exceeds the reference level, the comparator outputs a logical high ('1'); otherwise, it outputs a logical low ('0').

The combined output from all comparators forms a thermometer code—a binary sequence consisting of consecutive '1's followed by '0's. For instance, if the input lies between the 6th and 7th reference voltages, the first six comparators produce a '1', while the remaining comparators output '0'. This thermometer pattern is then fed into a digital encoder, which converts it into a 4-bit binary value that accurately represents the analog input level in digital form.

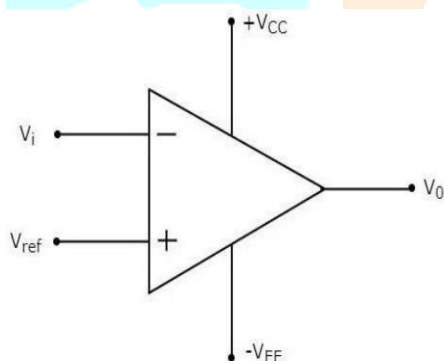


Fig No 4.1 Block Diagram of Comparator

Comparators play a vital role in the design of analog and mixed-signal systems, especially in high-speed applications such as Flash Analog-to-Digital Converters (ADCs). Fundamentally, a comparator evaluates two voltage inputs: one is the signal of interest (V_i), and the other is a reference level (V_{ref}). The circuit has two terminals—non-inverting (+) and inverting (—)—through which it receives these inputs.

When the voltage at the non-inverting terminal exceeds the voltage at the inverting terminal, the output rapidly transitions to a high state, approaching the positive supply rail ($+V_{CC}$). Conversely, if the inverting input is higher, the output drops to a low state, near ground or $-V_{EE}$, depending on the supply configuration. This sharp transition mimics binary logic behavior, effectively allowing the comparator to act as a one-bit analog-to-digital converter, producing a digital '1' or '0' based on the input comparison.

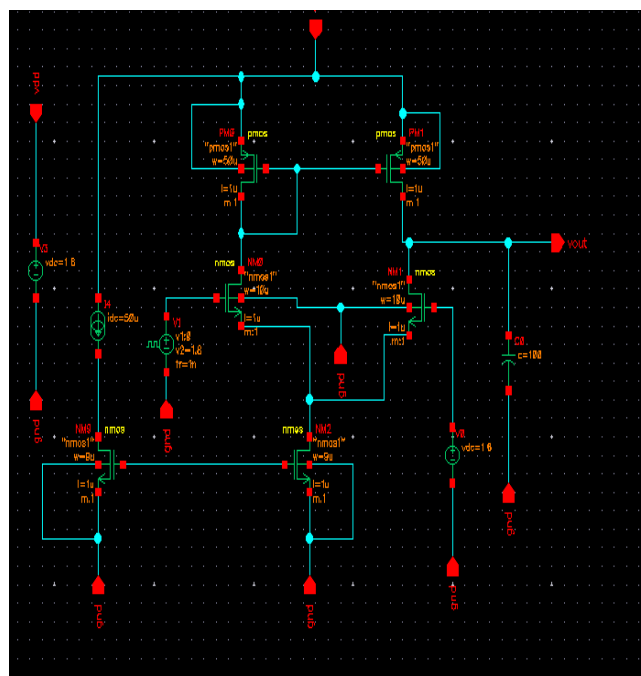


Fig No 4.2 Schematic of Comparator

Internally, a comparator circuit is commonly built around a differential amplifier configuration, using a matched pair of transistors—typically either BJTs or MOSFETs. This pair forms the core of the comparator, where it detects and amplifies small voltage differences between the two input signals. A bias current, typically supplied through a current mirror or current source, ensures proper operation, while the output gain is enhanced using either resistive or active loading.

The amplified signal is then passed through a high-gain output stage that rapidly drives the output to a defined logic level, enabling a crisp digital transition between high and low states. In the context of a 4-bit Flash ADC, an array of 15 comparators is employed. Each comparator receives the analog input and a unique reference voltage from a resistor ladder. Their outputs together form a thermometer code, which the encoder then translates into the corresponding 4-bit binary output that represents the input voltage level.

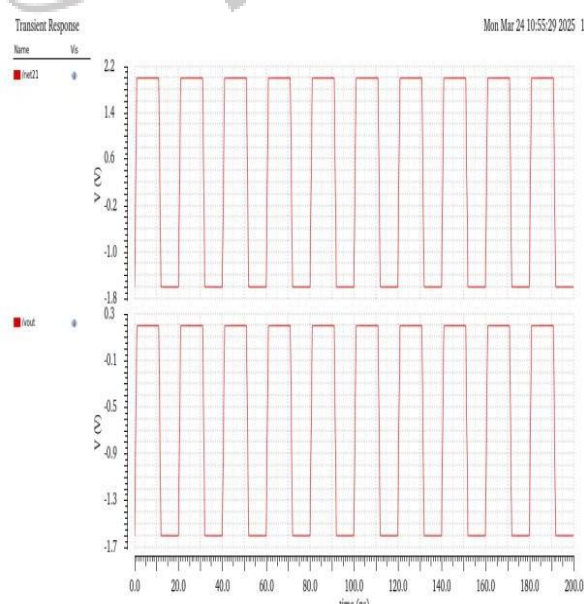


Fig No 4.3 Transient Response of Comparator

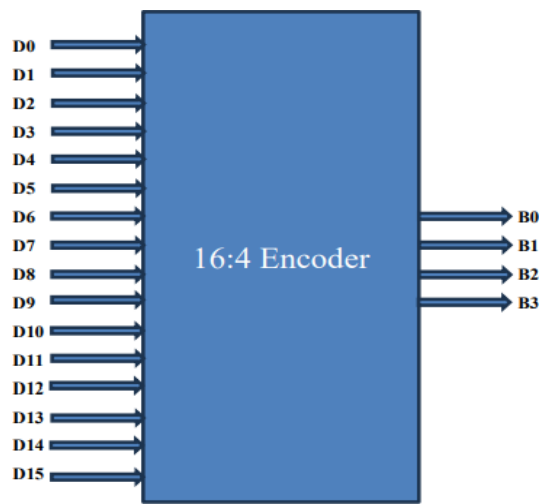


Fig No 4.4 Block Diagram of Encoder

In a 4-bit flash Analog-to-Digital Converter (ADC), the encoder plays a key role by translating the thermometer code from the comparator array into a 4-bit binary output. This type of ADC uses 15 comparators, each connected to a different reference voltage. The comparators produce a 15-bit thermometer code, which typically consists of consecutive '1's followed by '0's. The number of '1's indicates how many reference thresholds the input voltage has surpassed. For instance, if the input voltage exceeds six reference levels, the thermometer code would look like 111111000000000.

The encoder's primary function is to determine how many leading '1's are present in this code and convert that count into a 4-bit binary number. This binary output represents the digital value corresponding to the analog input voltage, ranging from 0000 (minimum level) to 1111 (maximum level).

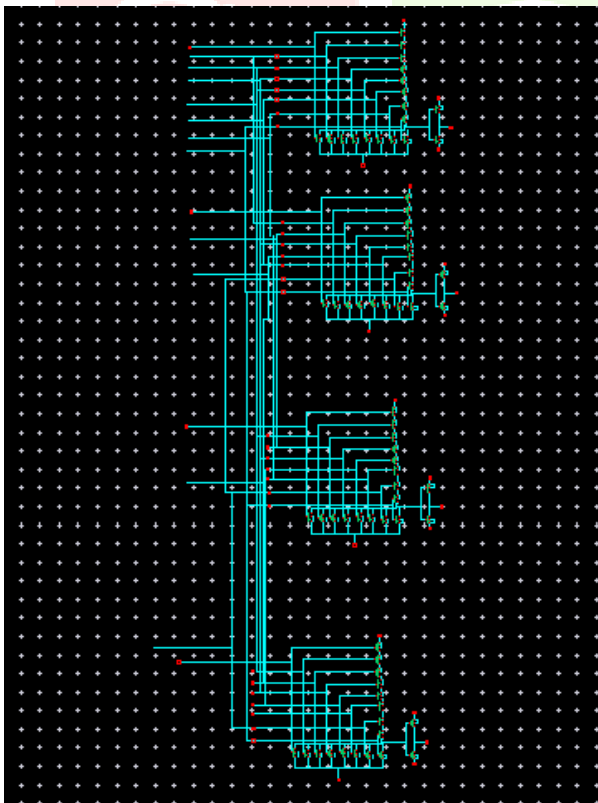


Fig No 4.5 Schematic of Encoder

In a 4-bit flash ADC designed using only schematics in Cadence Virtuoso, the encoder circuit plays a crucial role in converting the 15-bit thermometer code—generated by the array of comparators—into a 4-bit binary output. This thermometer code consists of a sequence of '1's followed by '0's, where the number of leading '1's corresponds to the input voltage level.

To implement this encoder at the schematic level, a priority encoder architecture is typically used. The design consists of combinational logic gates arranged to detect the position of the last '1' before the first '0' occurs. This is achieved by chaining logic stages that monitor each bit of the thermometer code and determine where the transition from '1' to '0' happens. Only the highest active bit is passed to the output logic, ensuring a valid binary count.

The final 4-bit binary output represents the quantized level of the analog input and must be optimized for speed and signal integrity. Special attention should be given to gate sizing, load balancing, and fan-out control to maintain the high-speed advantage of the flash ADC architecture.

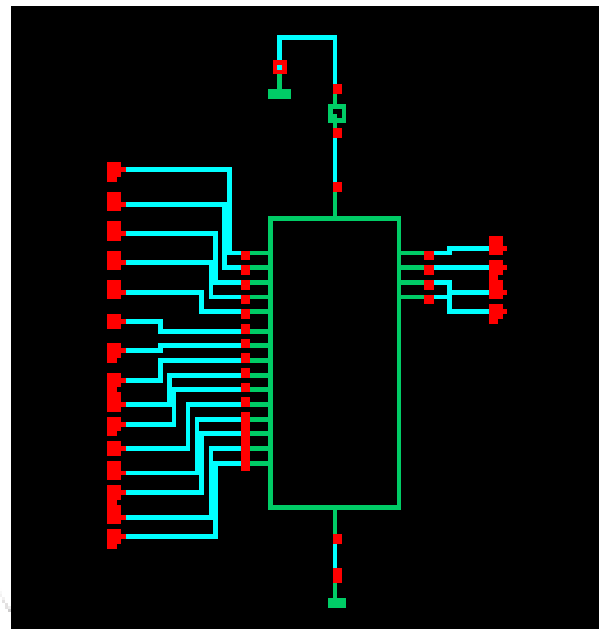


Fig No 4.6 Symbol of Encoder

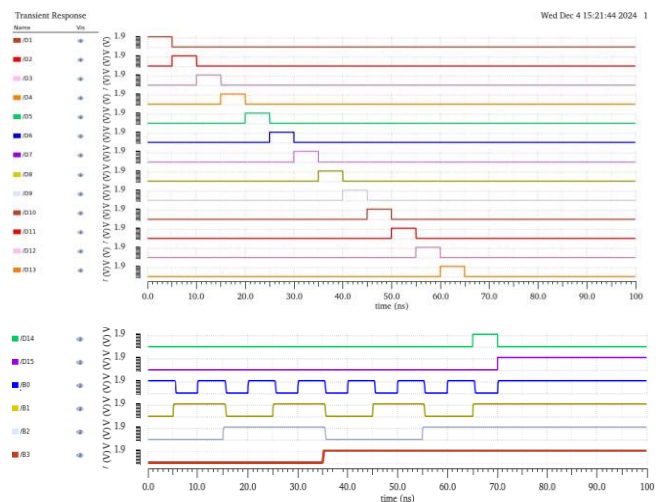


Fig No 4.7 Transient Response of Encoder

Finally, the 4-bit binary output is delivered as the digital representation of V_{in} . This architecture ensures extremely fast conversion because all comparisons happen in parallel. However, it also means that the number of comparators grows exponentially with resolution—requiring $2^n - 1$ comparators for an n -bit ADC—so this method is typically used for low-resolution, high-speed applications like video and radar signal processing.

V. RESULTS

A 4-bit flash ADC produces a 4-bit binary output that digitally represents the level of an analog input voltage. Since it can distinguish 16 discrete levels, the entire input range—from 0 V up to the reference voltage (V_{ref})—is divided into 16 uniform steps. Each step corresponds to a voltage interval of $V_{ref}/16$. For example, if V_{ref} is 5 V, each quantization step equals 0.3125 V.

When an input voltage (V_{in}) is applied, the ADC determines which interval it falls into and outputs the corresponding 4-bit binary code. So, if V_{in} is 2.5 V, which aligns with the 8th step, the ADC will generate the binary output 1000.

The conversion process begins with a bank of 15 comparators, each comparing V_{in} to a fixed reference voltage level. The outputs of these comparators form a thermometer code—an array of '1's followed by '0's depending on how many thresholds V_{in} has crossed. This thermometer code is then passed to an encoder, which translates it into the final binary output.

Flash ADCs are particularly known for their speed. Because all comparisons and the encoding logic operate in parallel, they offer extremely fast conversion times, making them ideal for high-performance applications such as video processing, real-time signal acquisition, and other bandwidth-intensive tasks.

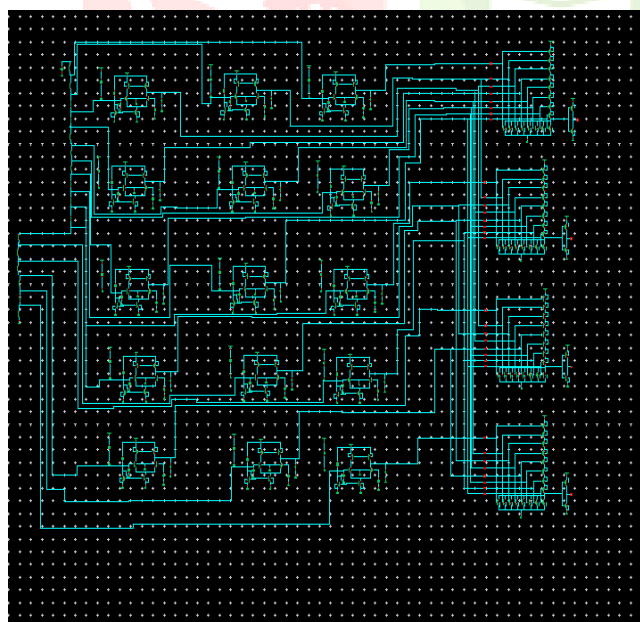


Fig No 5.1 Schematic of 4-Bit Flash ADC

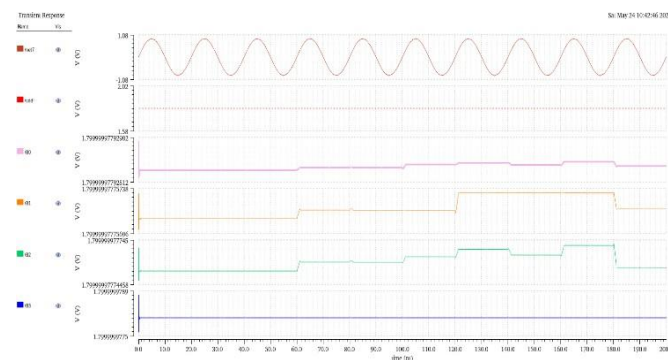


Fig No 4.7 Transient Response of 4-Bit Flash ADC

REFERENCES

- [1] M. Njinowa, H. Bui and F. Boyer, "Novel Threshold-Based Standard-Cell Flash ADC," *Circuits and Systems*, Vol. 3, No. 1, pp. 29-34, January 2012.
- [2] S. Bandyopadhyay, D. Mukherjee, and R. Chatterjee, "Design of two-stage CMOS operational amplifier in 180nm technology with low power and high CMRR," *Int. J. Recent Trends Eng. Technol.*, vol. 11, June 2014.
- [3] G. L. Madhumati, M. K. R. Rao and M. Madhavilatha, "Comparison of 5-bit Thermometer-to-Binary Decoders in 1.8V 0.18 μ m CMOS Technology for Flash ADCs," *Int. Conf. Signal Process. Syst.*, pp. 1–8, Aug. 2024.
- [4] M. J. Kaur and S. Kansal, "Study of Various ADCs and Compare Their Performance and Parameters," *Int. J. Adv. Eng. Res. Technol.*, vol. 3, no. 3, 2015.
- [5] M. Das et al., "Design of Ultra Low Power Novel 3-Bit Flash ADC in 45nm CMOS Technology," *ICSTM*, 2015.
- [6] S. Hussain, R. Kumar, and G. Trivedi, "A novel low-power high-speed BEC for 2 GHz sampling rate flash ADC in 45 nm technology," *Proc. Int. Symp. Nanoelectron. Inf. Syst. (INIS)*, 2017.
- [7] A. P. Chavan et al., "Design of a 1.5-V 4-bit flash ADC using 90 nm technology," *Int. J. Eng. Adv. Technol.*, no. 2, 2012.
- [8] H. M. Muruges and D. Nagesh, "Implementation of a 4-bit two-step flash ADC using 180 nm technology," *Int. J. Technol. Res. Eng.*, vol. 3, 2016.
- [9] S. Kumar and R. Yadav, "Design of a 4-bit flash ADC using 180 nm technology," *Int. J. Sci. Res. Dev. (IJSRD)*, vol. 5, 2017.
- [10] S. T. Yamamoto et al., "A mixed-signal 0.18 μ m CMOS SoC for DVD systems with 432-Msample/s PRML read channel and 16-Mb embedded DRAM," *IEEE J. Solid-State Circuits*, vol. 36, pp. 1785–1794, Nov. 2001.